



# **MIPS Single-Cycle Final Project**

**Abdelrahman Ahmed Nabil Ahmed Mahmoud**

221000309 - Class(3)

**Supervised by:**

Dr/Marwa ElShenawy


Eng/Rama Hamdy

# Project Overview

This project tackles VHDL implementation of a simple MIPS processor which executes each instruction in a singular clock cycle.


This processor is designed to execute two main types of instruction:

- 1- R-Type
- 2- I-Type

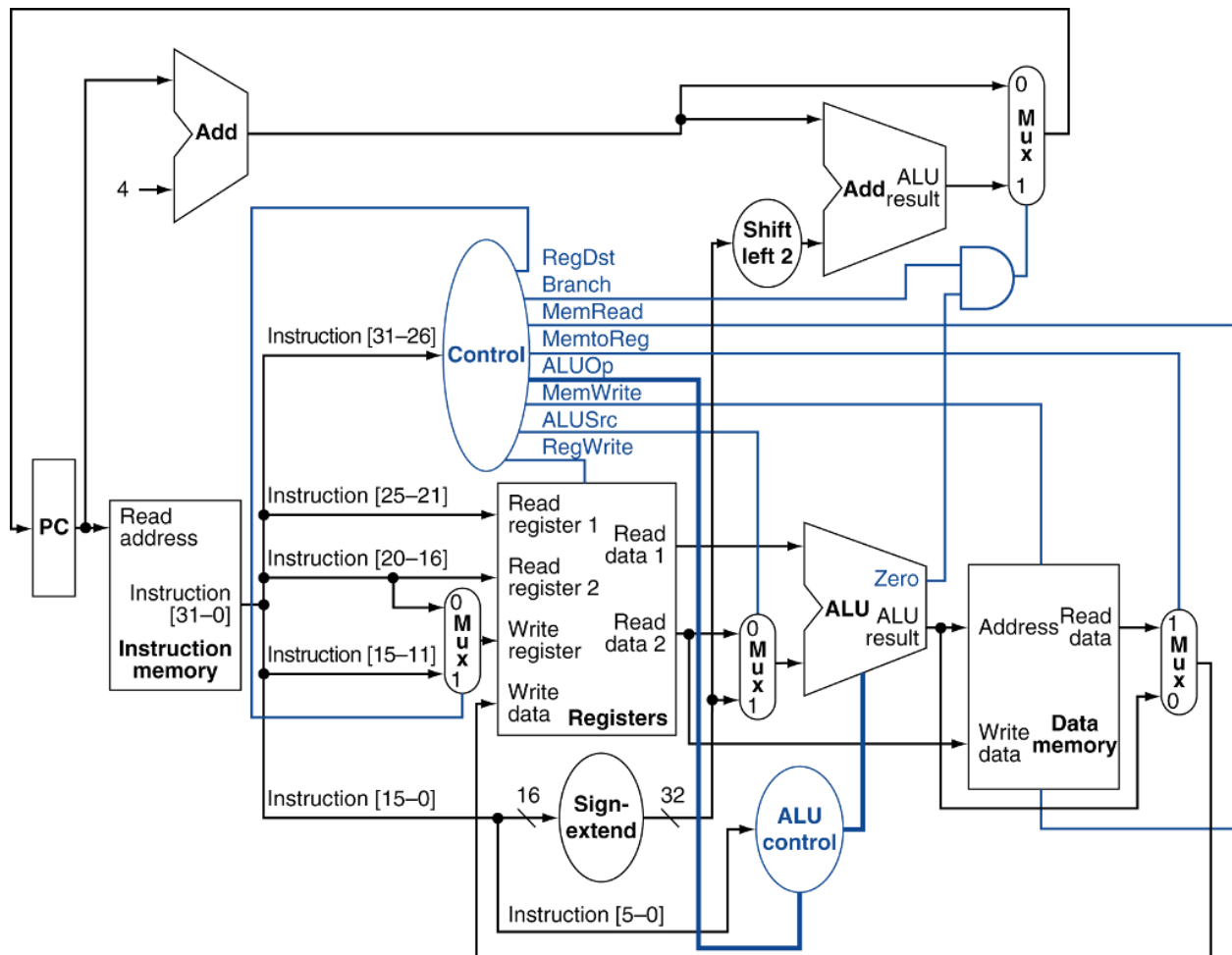

All used components:

#### Hierarchy

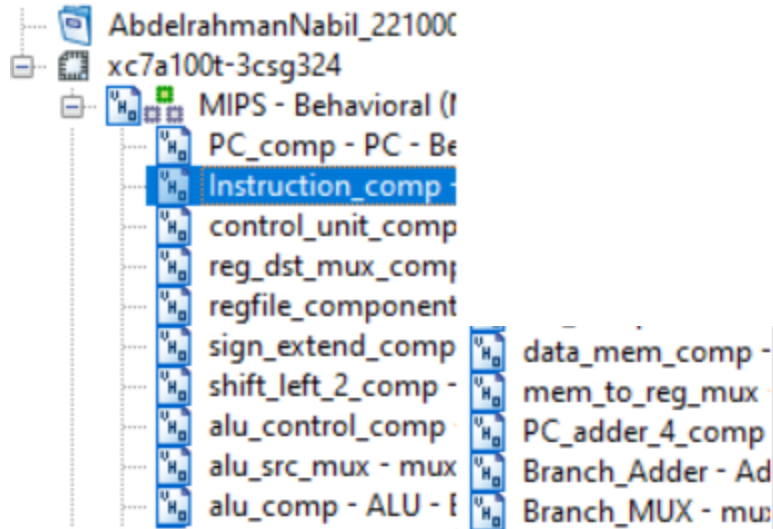

First and foremost, a common starting point between all instructions is

- Fetching the instruction : At the rise of the clock cycle, the PC is passed as input to the instruction memory, where it serves as an address to fetch my instruction. The output is the actual 32 bits that represent the instruction itself.


Second of all the function is decoded to:

- Opcode to decide control signals
- Inputs to the register file(rs,rt,rd)
- Input to sign extend (in case of immediate value)
- Input to ALU Control (function field)
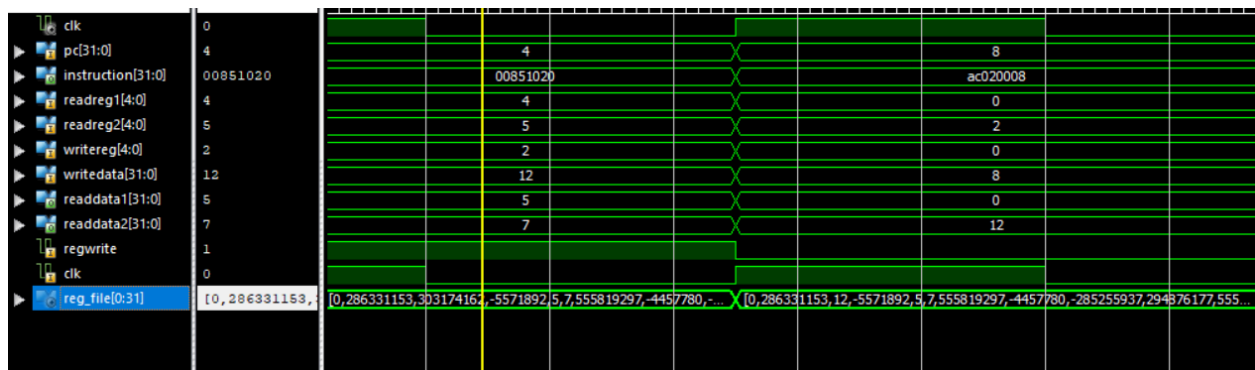
# R-Type Instructions


For R-type instructions such as *add*, the following occurs:

- 1- rs and rt are read registers
- 2- rd is selected to be the write register from the mux to be the write register as the control signal RegDst is 1
- 3- rs and rt are inputs to the ALU, where rt is selected and not an immediate value due to the value of the control signal ALUSrc.
- 4- Finally the result is calculated via the ALU
- 5- It is selected in the final mux to be the write data, and then it is written back to the register.




In this screenshot , data from registers (4 and 5) are added and written into register(2). The output is (5+7 = 12) and it is evident in the next clock cycle where index(2) in the register file has in fact changed.

## Memory Manipulation Functions

 


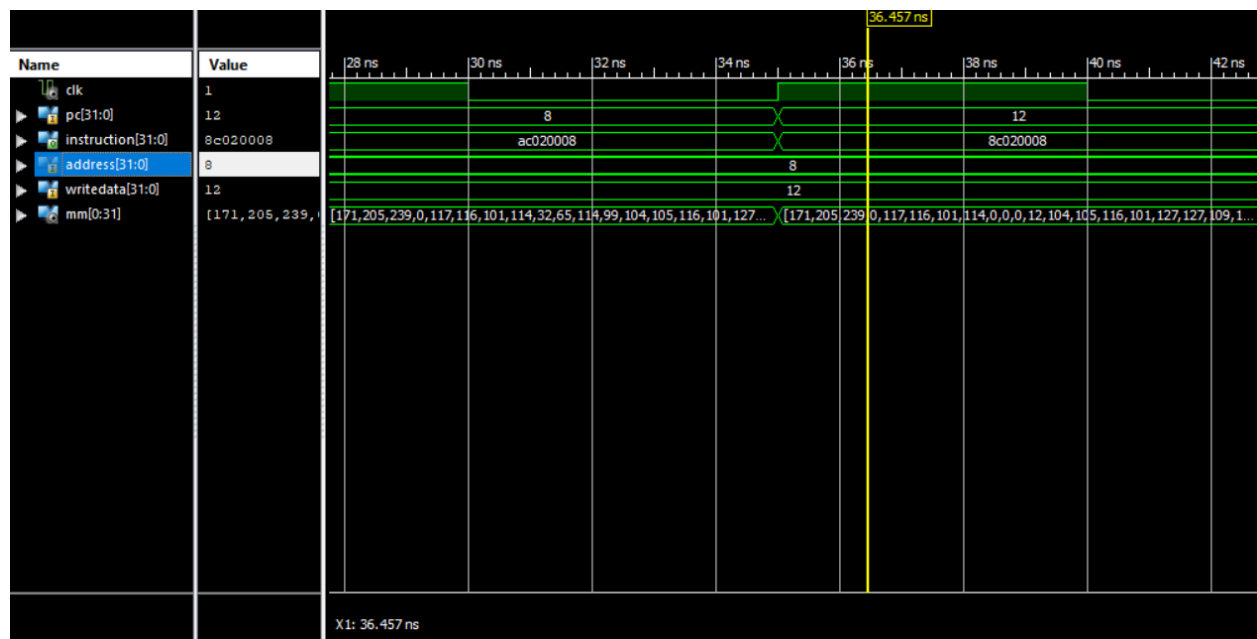The address is calculated by adding rs to the immediate value. In this case zero register containing zero is added to 8, giving the address of 8.



As can be observed here, the indexes 8 through 11 were used for writing the data, which is because of the byte-addressable memory.

## Branch Instructions

 

For the branch instruction, it was shown that the branch control signal is in fact 0 ; however , since zero flag from ALU isnt 1 the condition isnt fulfilled completely in this case, and no branch occurs. When tested with equal values, it was shown that the PC skipped the next +4 and moved straight to 20 instead of 16.

# Mapping Code

Attached here is the picture for the port mapping code in order to define the MIPS datapath, using the signals defined in the MIPS architecture, to connect each component to the other.

```
201 ----- Fetching Instruction -----
202 PC_comp: PC port map (CLK,NextPC,InstructionAddress);
203 Instruction_comp: instruction_file port map(InstructionAddress,CLK,Instruction);
204 -----
205
206
207 ----- Decoding Instruction -----
208 Opcode <- Instruction(31 downto 26);
209 control_unit_comp: control_unit port map (Opcode,RegDst,AluSrc, MemtoReg,RegWrite,MemRead,MemWrite,Branch,ALUOp1,AL
210 ALUOp <- ALUOp1 & ALUOp0;
211 -----
212
213 ----- Dividing Instruction -----
214 rs <- Instruction(25 downto 21);
215 rt <- Instruction(20 downto 16);
216 rd <- Instruction(15 downto 11);
217 SignExtendIn <- Instruction(15 downto 0);
218 ALUControl_In <- Instruction(5 downto 0);
219 -----
220
221 ----- Reg_Dst + Register File -----
222 reg_dst_mux_comp : reg_dst_mux port map(rt,rd,RegDst,RegDst_Output);
223 regfile_component : reg_file port map(rs,rt,RegDst_Output,RegWriteData,ReadData1,ReadData2,RegWrite,CLK);
224 -----
225
226
227 ----- Sign extend and Shift left 2 -----
228 sign_extend_comp : sign_extend port map(SignExtendIn,SignExtendOut);
229 shift_left_2_comp : shifter_32_32 port map(SignExtendOut,ShiftLeftOut);
230 -----
231
232 ----- ALU Control & ALU -----
233 alu_control_comp : ALU_Control port map(ALUOp,ALUControl_In,ALUControl_Out);
234 ALU_In1 <- ReadData1;
235 alu_src_mux : mux_2_x_1 port map(ALUSrc,ReadData2,SignExtendOut,ALU_In2);
236 alu_comp : ALU port map(ALU_In1,ALU_In2,ALUControl_Out,ALU_Out,Zero);
237 -----
238
239 ----- Data Memory -----
240 data_mem_comp : mem_file port map(ALU_Out,ReadData2,MemWrite,MemRead,CLK,MemReadData);
241 mem_to_reg_mux: mux_2_x_1 port map(MemtoReg,ALU_Out,MemReadData,RegWriteData);
242 -----
243
244 ----- Adders -----
245 PC_adder_4_comp : PC_adder_4 port map (InstructionAddress,PCAdder_Out);
246 Branch_Adder : Adder port map (PCAdder_Out, ShiftLeftOut,BranchAdder_Out);
247 Branch_MUX : mux_2_x_1 port map (Branch AND Zero,PCAdder_Out, BranchAdder_Out,NextPC);
248 -----
249
250
```